

Report 03

Filippo Nevi - VR458510

October 2020

1 Design choices

1.1 Process style


I've chosen to implement the Fixed-point Multiplier using the **sequential synchronous** style because it represents a Final State Machine with (in my case) five states, so it needs a clock signal to synchronize the circuit.

1.2 Datatypes

I've only used BIT, UNSIGNED and INTEGER datatypes to model this circuit because these types are synthesizable, and since the fixed-point multiplication's algorithm is simply an integer multiplication with, at the end of it, the addition of the point at half of the product, I implemented this circuit without considering the point. The operands and result are converted in their rational form in the Tcl console when executing *stimuli.tcl*.

2 Simulation waveforms

2.1 Testbench

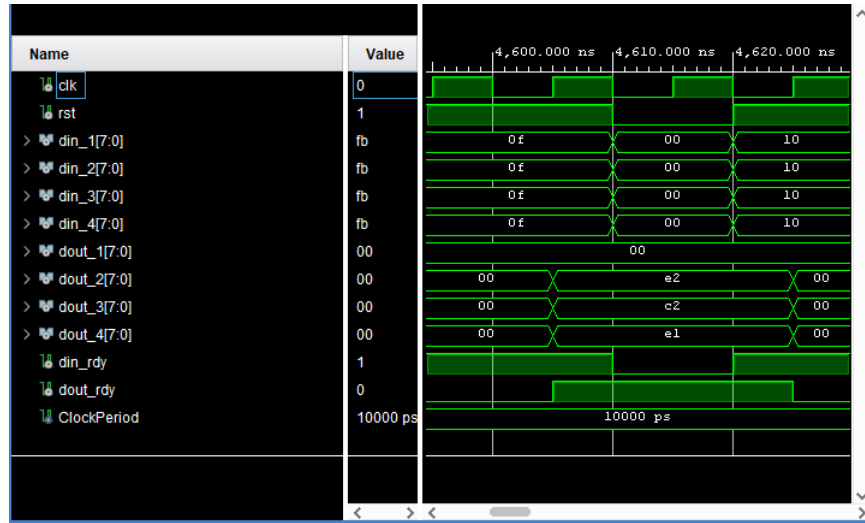

These waveforms show that all the four input signals **din_1**, **din_2**, **din_3**, **din_4** have the same hexadecimal value 0F.

This integer multiplication is 0F0F·0F0F, and the result signals are


- **dout_1** = 00
- **dout_2** = E2
- **dout_3** = C2
- **dout_4** = E1

Converting the numbers in the fixed-point notation, we find out that the operation is:

$$15.05859375 \cdot 15.05859375 = 226.7612457275390625$$

We can also notice that the signal **dout_rdy** has positive value when the output signals are showing the results, while **din_rdy** and **rst** have negative value because the input signals are being reset.

2.2 Stimuli.tcl

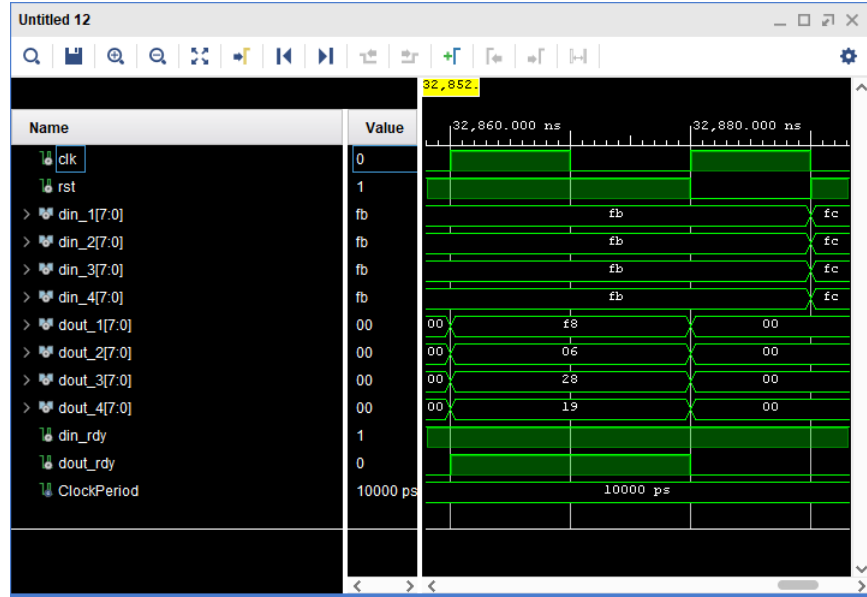

In the image above, we can see that all the four input signals have the value FB. The multiplication is FBFB·FBFB, and the result signals are the values at time 32860ns:

- dout_1 = F8
- dout_2 = 06
- dout_3 = 28
- dout_4 = 19

Converting the numbers in Fixed-point notation, the operation is:

$$251.98046875 \cdot 251.98046875 = 63494.15663146973$$